

**North South University**  
Department of Electrical & Computer Engineering


**Assessment 03**

**Name** : Fariha Nur Hasin

**ID** : 1912148642

**Course** : CSE231.1

## Constructing a Sequential Circuit using JK , D and T Flip-Flops

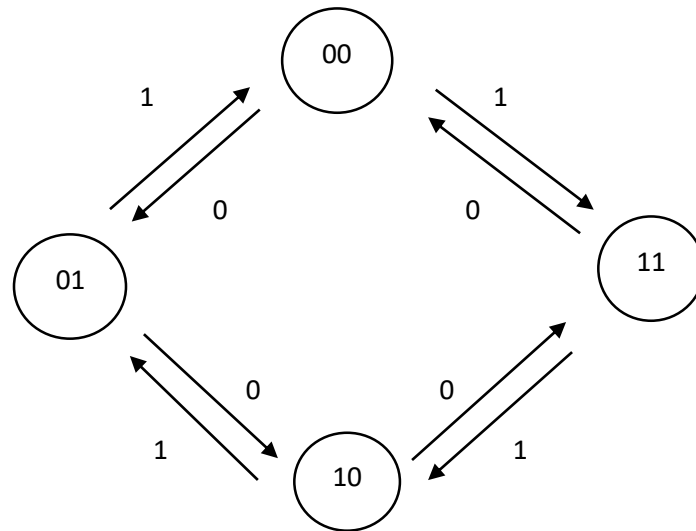

**Figure : State Diagram for a Synchronous Sequential Circuit**

Number of input = 1 (X)

Number of state variable = 2 (A,B)

When input  $x = 0$ , loop will go anti-clock wise.

When input  $x = 1$ , loop will go clock wise.

## Constructing a Sequential Circuit using D Flip-Flops :

Previous State		Input	Next state		Flip-Flop Input Function	
A	B	X	A	B	D <sub>A</sub>	D <sub>B</sub>
0	0	0	0	1	0	1
0	0	1	1	1	1	1
0	1	0	1	0	1	0
0	1	1	0	0	0	0
1	0	0	1	1	1	1
1	0	1	0	1	0	1
1	1	0	0	0	0	0
1	1	1	1	0	1	0

**BX**

**A**

	1		1
1		1	


**BX**

**A**

1	1		
1	1		

$$D_A = AB'X' + A'B'X + A'BX' + ABX$$


$$D_B = B'$$

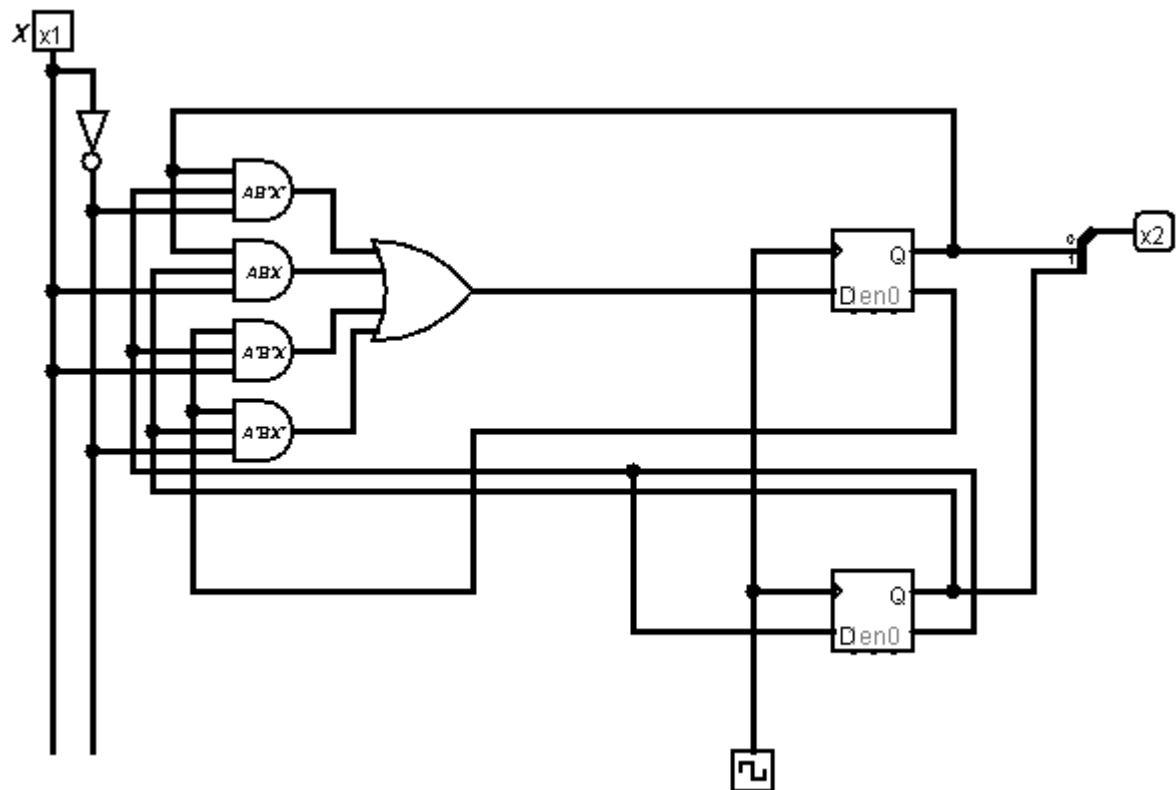


**Figure- D Flip-Flop**

## Constructing a Sequential Circuit using T Flip-Flops :


Previous State		Input	Next state		Flip-Flop Input Function	
A	B	X	A	B	T <sub>A</sub>	T <sub>B</sub>
0	0	0	0	1	0	1
0	0	1	1	1	1	1
0	1	0	1	0	1	1
0	1	1	0	0	0	1
1	0	0	1	1	0	1
1	0	1	0	1	1	1
1	1	0	0	0	1	1
1	1	1	1	0	0	1

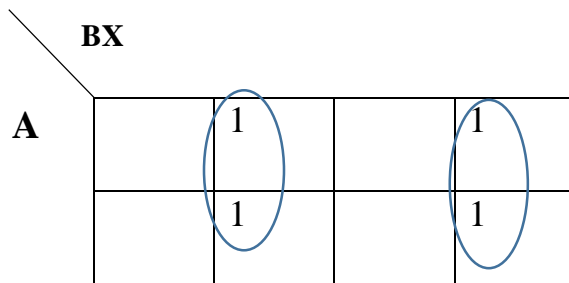

$$T_A = B'X + BX'$$

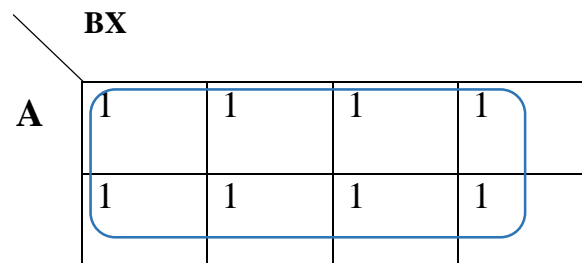

$$T_B = 1$$

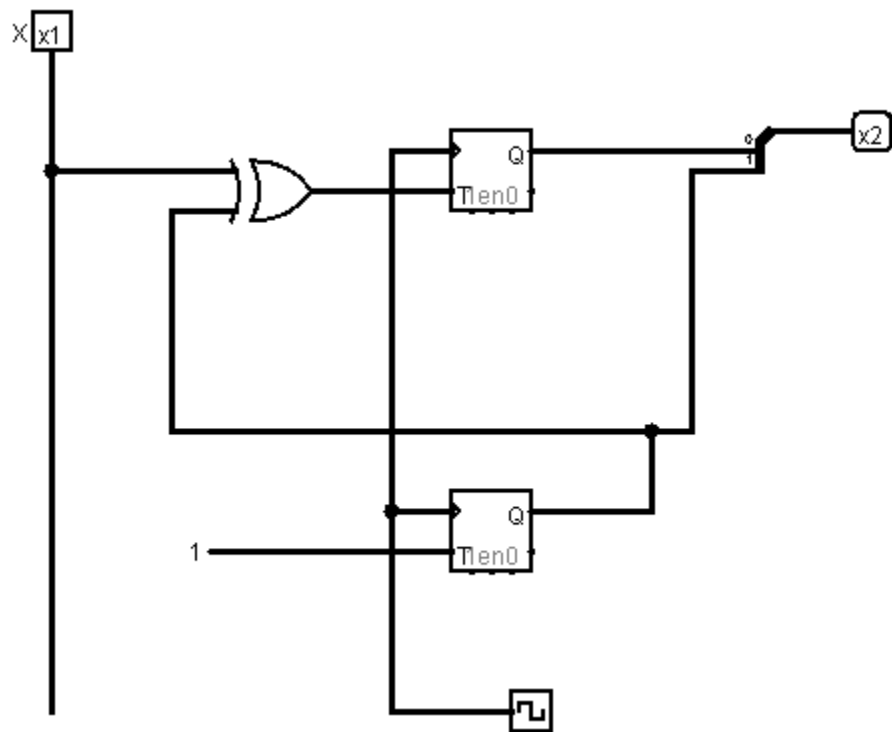

**Figure – T flip-flop**

## Constructing a Sequential Circuit using JK Flip-Flops :

Previous State		Input	Next state		Flip-Flop Input Function			
A	B	X	A	B	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>
0	0	0	0	1	0	x	1	x
0	0	1	1	1	1	x	1	x
0	1	0	1	0	1	x	x	1
0	1	1	0	0	0	x	x	1
1	0	0	1	1	x	0	1	x
1	0	1	0	1	x	1	1	x
1	1	0	0	0	x	1	x	1
1	1	1	1	0	x	0	x	1

**BX**

**A**

	1		1
X	X	X	X

$$J_A = B'X + BX'$$

**BX**

**A**

X	X	X	X
	1		1

$$K_A = B'X + BX'$$

**BX**

**A**

1	1	X	X
1	1	X	X


$$J_B = 1$$

**BX**

**A**

X	X	1	1
X	X	1	1

$$K_B = 1$$

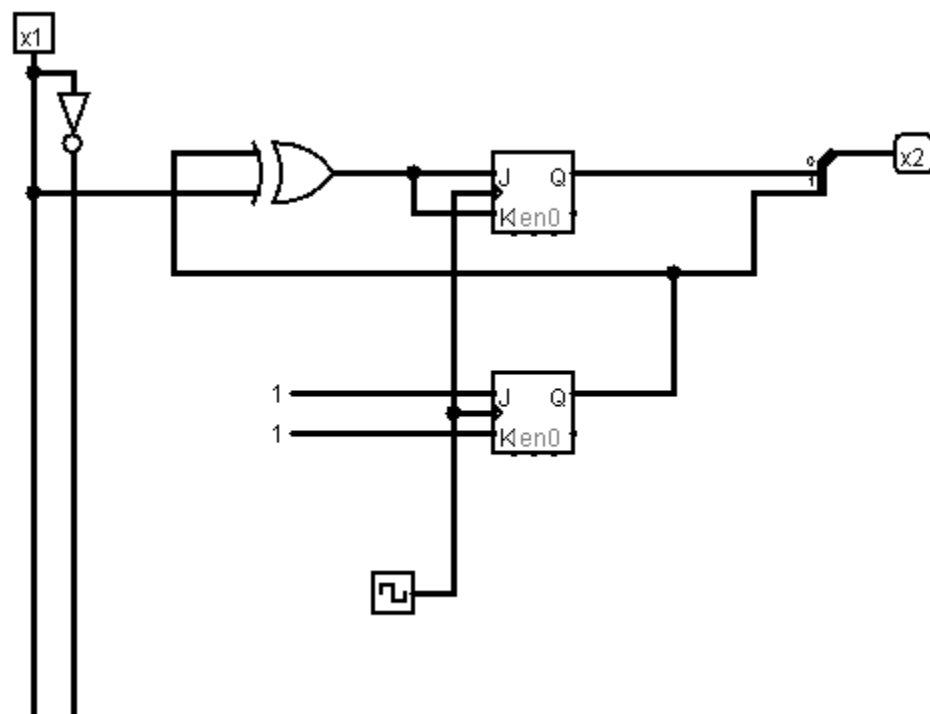

**Figure- JK Flip-Flop**